

## Power-Up Considerations

### INTRODUCTION

When powering up all microcontrollers it is necessary for the power supply voltage to traverse voltage ranges where the device is not guaranteed to operate before the power supply voltage reaches its final state. Since some circuits on the device (logic) will start operating at voltage levels lower than other circuits on the chip (memory), the device may power-up in an unknown state. To guarantee that the device starts up in a known state, it is necessary that it contain a power-up reset circuit. PIC16C5X microcontrollers are equipped with on-chip power-on reset circuitry, which eliminates the need for external reset logic. This circuit will function in most power-up situations where  $V_{CC}$  rise time is fast enough (50 ms or less). This application note describes the typical power-up sequence for PIC16C5X microcontrollers. Methods of assuring reset on power-up and after a brownout are discussed and simple, low cost external solutions are discussed for power-up situations where the PIC16C5X's internal circuitry cannot provide the reset.

### POWER-UP SEQUENCE


The PIC16C5X incorporates complex power-on reset (POR) circuitry on-chip which provides solid, reliable internal chip reset for most power-up situations. To use this feature, the user merely needs to tie MCLR to VDD. A simplified block diagram of the on-chip reset circuitry is shown in Figure 1. On power-up, the reset latch and

the start-up timer are reset to appropriate states by the power-on reset (POR). The start-up timer will begin counting once it detects MCLR to be high (i.e., external chip reset goes inactive). After the time-out period, which is typically 18 ms long, the timer will reset the reset latch and thus end the on-chip reset signal.

Figures 2 and 3 are two power-up situations with relative fast rise time on VDD. In Figure 1, VDD is stable when MCLR is brought high (i.e., reset pulse is being provided by external source). The chip actually comes out reset about  $t_{OST}$  ms after that, where  $t_{OST}$  = oscillator start-up timer. (The timer is called oscillator start-up timer because the time-out was incorporated primarily to allow the crystal oscillator to stabilize on power-up.) In Figure 3, the MCLR and VDD are tied together and clearly the on-chip reset mechanism is being utilized. The VDD is stable before the start-up timer expires and there is no problem with proper reset.

Figure 4, where VDD rise time is much greater than  $t_{OST}$  (typically 18 ms) clearly is the potentially problematic situation. The POR (power-on reset) pulse comes when VDD is about 1.5V. Most CMOS logic, including the start-up timer starts functioning between 1.5V to 2.0V. When the start-up timer starts times out, the chip reset is ended and the chip attempts to execute. If by this time the VDD has reached VDD MIN value, then all circuits are guaranteed to function correctly and power-up reset is successful. If, however, the VDD slope was too slow and had not reached VDD MIN, then the chip may or may not function properly.

**FIGURE 1 - PIC16C5X INTERNAL RESET CIRCUIT**

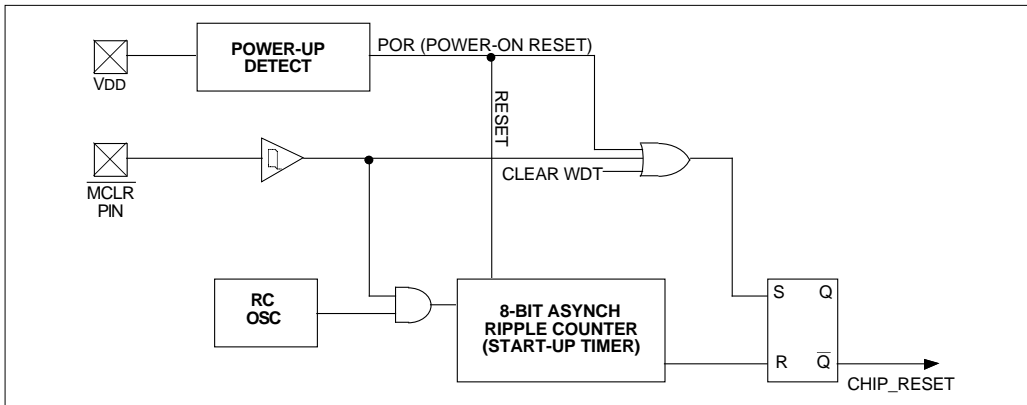

# Power-Up Considerations

FIGURE 2 - EXTERNAL RESET PULSE

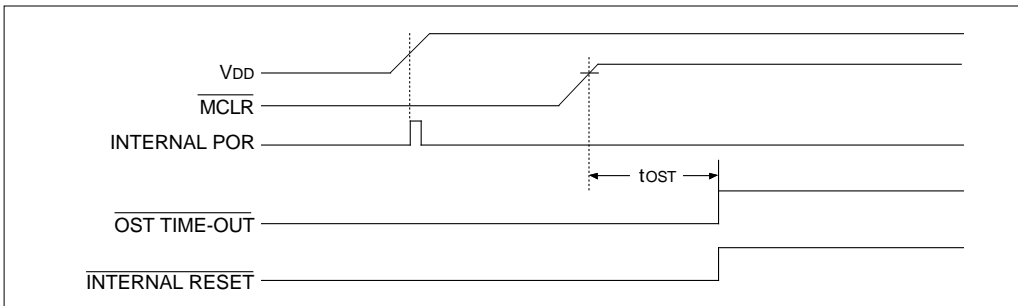


FIGURE 3 - INTERNAL RESET ( $V_{DD}$  AND  $\overline{MCLR}$  TIED TOGETHER)


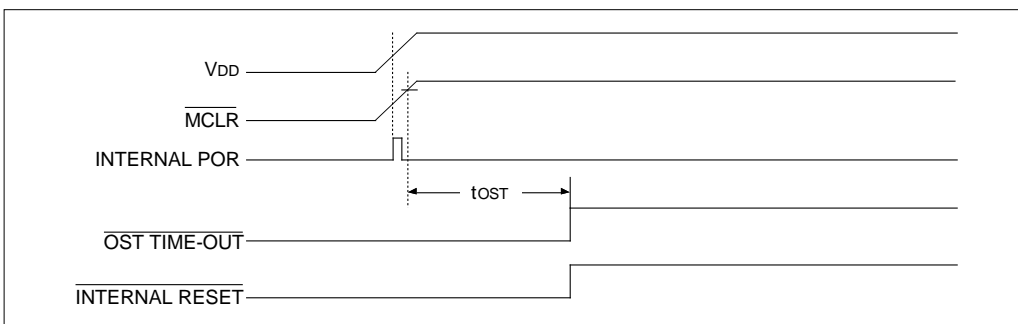



FIGURE 4 - INTERNAL RESET ( $V_{DD}$  AND  $\overline{MCLR}$  TIED TOGETHER): SLOW  $V_{DD}$  RISE TIME

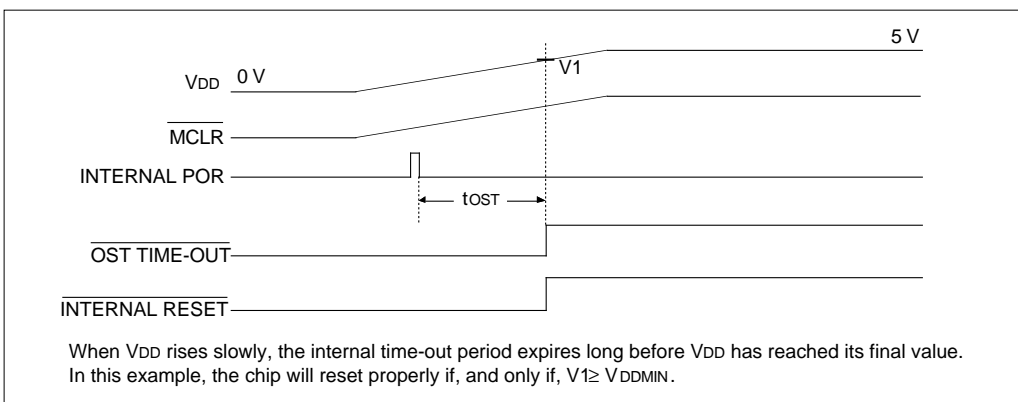

## EXTERNAL POWER-ON RESET CIRCUIT

To use power supplies with slow rise times it is necessary to use an external power-on reset circuit such as the one shown in Figure 5. This circuit uses an external RC to generate the reset pulse. The time constant of the RC should be long enough to guarantee that the reset pulse is still present until V<sub>DD</sub> has reached V<sub>DD min</sub>. R should be 40K or less to guarantee that the MCLR will pull to within 0.2 volts of V<sub>DD</sub>. (since the leakage spec on MCLR is ±5 µA, a resistor larger than 40K may cause input high voltage on this pin to be less than V<sub>DD</sub> - 0.2V, the required spec). The diode D is used to rapidly discharge the capacitor on power-down. This is very important as a power-up reset pulse is needed after a short power-down (less than the time constant of RC) or after a power spike. The resistor R1 protects against high current flowing into MCLR pin from fully charged capacitor C in the event MCLR pin breakdown is induced through ESD or EOS. The circuit, however, does not protect against brown-out situations where the power does not drop to zero, but merely dips below V<sub>DD MIN</sub>. In such a situation, voltage at the MCLR pin will not go low enough (i.e., below V<sub>IL</sub>) to guarantee a reset pulse. The following section presents an example circuit to protect against such brown-outs.


**FIGURE 5 - EXTERNAL POWER-ON RESET CIRCUIT**

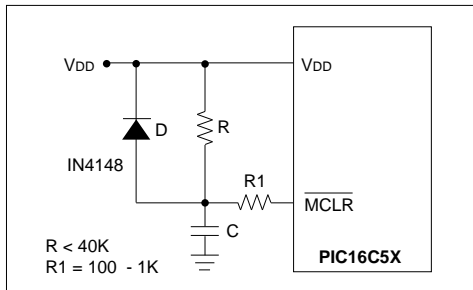


## BROWNOUT PROTECTION

In many applications it is necessary to guarantee a reset pulse whenever V<sub>DD</sub> is less than V<sub>DD min</sub>. This can be accomplished using a brownout protection circuit such as the one shown in Figure 6. This is a simple circuit that causes a reset pulse whenever V<sub>DD</sub> drops below the zener diode voltage plus the V<sub>be</sub> of Q1. A 3.3 volt zener will produce a reset pulse whenever V<sub>DD</sub> drops below about 4 volts. This circuit has a typical accuracy of about ±100 mV. A less expensive, albeit less precise, brown-out circuit is shown in Figure 7. Transistor Q1 turns off when  $V_{be} = V_{DD} \cdot R1 / (R1 + R2)$  falls below 0.7 V allowing R3 to pull down MCLR input.

**FIGURE 6 - BROWNOUT PROTECTION CIRCUIT**

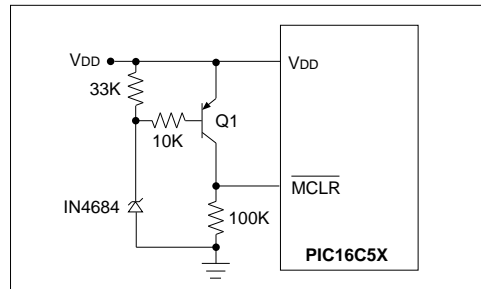

**FIGURE 7 - BROWNOUT PROTECTION CIRCUIT**

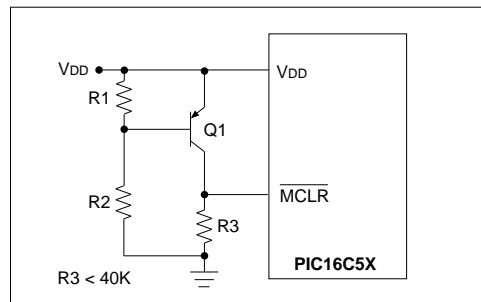

Author: Sumit Mitra  
Logic Products Division

# Power-Up Considerations

---

NOTES:

---

---

# WORLDWIDE SALES & SERVICE

---

---

## AMERICAS

### Corporate Office

Microchip Technology Inc.  
2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 602 786-7200 Fax: 602 786-7277  
Technical Support: 602 786-7627  
Web: <http://www.mchip.com/microhip>

### Atlanta

Microchip Technology Inc.  
500 Sugar Mill Road, Suite 200B  
Atlanta, GA 30350  
Tel: 770 640-0034 Fax: 770 640-0307

### Boston

Microchip Technology Inc.  
5 Mount Royal Avenue  
Marlborough, MA 01752  
Tel: 508 480-9990 Fax: 508 480-8575

### Chicago

Microchip Technology Inc.  
333 Pierce Road, Suite 180  
Itasca, IL 60143  
Tel: 708 285-0071 Fax: 708 285-0075

### Dallas

Microchip Technology Inc.  
14651 Dallas Parkway, Suite 816  
Dallas, TX 75240-8809  
Tel: 214 991-7177 Fax: 214 991-8588

### Dayton

Microchip Technology Inc.  
35 Rockridge Road  
Englewood, OH 45322  
Tel: 513 832-2543 Fax: 513 832-2841

### Los Angeles

Microchip Technology Inc.  
18201 Von Karman, Suite 455  
Irvine, CA 92715  
Tel: 714 263-1888 Fax: 714 263-1338

### New York

Microchip Technology Inc.  
150 Motor Parkway, Suite 416  
Hauppauge, NY 11788  
Tel: 516 273-5305 Fax: 516 273-5335

## AMERICAS (continued)

### San Jose

Microchip Technology Inc.  
2107 North First Street, Suite 590  
San Jose, CA 95131  
Tel: 408 436-7950 Fax: 408 436-7955

## ASIA/PACIFIC

### Hong Kong

Microchip Technology  
Unit No. 3002-3004, Tower 1  
Metroplaza  
223 Hing Fong Road  
Kwai Fong, N.T. Hong Kong  
Tel: 852 2 401 1200 Fax: 852 2 401 3431

### Korea

Microchip Technology  
168-1, Youngbo Bldg. 3 Floor  
Samsung-Dong, Kangnam-Ku,  
Seoul, Korea  
Tel: 82 2 554 7200 Fax: 82 2 558 5934

### Singapore

Microchip Technology  
200 Middle Road  
#10-03 Prime Centre  
Singapore 188980  
Tel: 65 334 8870 Fax: 65 334 8850

### Taiwan

Microchip Technology  
10F-1C 207  
Tung Hua North Road  
Taipei, Taiwan, ROC  
Tel: 886 2 717 7175 Fax: 886 2 545 0139

## EUROPE

### United Kingdom

Arizona Microchip Technology Ltd.  
Unit 6, The Courtyard  
Meadow Bank, Furlong Road  
Bourne End, Buckinghamshire SL8 5AJ  
Tel: 44 0 1628 851077 Fax: 44 0 1628 850259

### France

Arizona Microchip Technology SARL  
2 Rue du Buisson aux Fraises  
91300 Massy - France  
Tel: 33 1 69 53 63 20 Fax: 33 1 69 30 90 79

### Germany

Arizona Microchip Technology GmbH  
Gustav-Heinemann-Ring 125  
D-81739 Muenchen, Germany  
Tel: 49 89 627 144 0 Fax: 49 89 627 144 44

### Italy

Arizona Microchip Technology SRL  
Centro Direzionale Colleoni  
Palazzo Pegaso Ingresso No. 2  
Via Paracelso 23, 20041  
Agrate Brianza (MI) Italy  
Tel: 39 039 689 9939 Fax: 39 039 689 9883

## JAPAN

Microchip Technology Intl. Inc.  
Benex S-1 6F  
3-18-20, Shin Yokohama  
Kohoku-Ku, Yokohama  
Kanagawa 222 Japan  
Tel: 81 45 471 6166 Fax: 81 45 471 6122

9/22/95

All rights reserved. © 1995, Microchip Technology Incorporated, USA.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights. The Microchip logo and name are registered trademarks of Microchip Technology Inc. All rights reserved. All other trademarks mentioned herein are the property of their respective companies.